

## EXTENDED SEVEN-SEGMENT DECODER/USING GIT

Lab01

**Otieno Maurice (Scribe)**

Daniel Hayes

31/10/2023

### **Introduction:**

The NEXY'S A7 100T printed circuit board provided in the lab has a seven-segment display. This display consists of eight digits driven by a common anode signal and each digit has seven segments made of LED lamps connected in a particular manner. This arrangement of LEDs allows us to display information depending on the signals the display receives. Each digit can display a range of characters from 0 TO F and characters such as P and C. Each digit is also supplied with a decimal point to its right end. Displaying information on all or some of the LEDs utilizes a time-multiplexed approach in which the anode signal to only one of the digits is enabled at a given time. The display on the NEXY'S A7 100T board uses active low rather than active high signals to drive this display. The board allows us to interface designs written in an HDL such as system Verilog or VHDL with the display by specifying the constraints written in tool command language.

In this lab we focused on driving only one digit of the seven-segment display. The CAD software used is for simulation and optimization was Vivado. We modelled the desired behavior in system Verilog and wrote a test bench to check that the described behavior is consistent with the desired behavior. We then synthesized the design, implemented it, routed the PCB and generated bitstream. We programmed the board with the bitstream and made observations.

We also learnt how to use the git version control system to store our code.

The code for all our designs can be found at

[https://github.com/otienomaurice1/ece212\\_alex\\_maurice.git](https://github.com/otienomaurice1/ece212_alex_maurice.git)

### **Design:**

#### 1. Design specifications:


- The design would interface with the last digit of the 8-digit seven-segment display for input and SWITCHES 0 TO 6 for output on the nexys100t printed circuit board.
- All elements of the design will be combinational
- The digit should have the ability to:
  - a.) Turn off both the display and the decimal point
  - b.) Display a minus sign on the display
  - c.) Display any of the digits from 0 to 9
  - d.) Display the characters A, C, F and P.

#### 2. Design implementation


- The overall design of the extended seven-segment controller utilized a top module named `sevensseg_ext_top`. This module consists of a seven-bit input named `data`, a single-bit output named `dp_n`, a seven-bit output named `segs_n` and an eight-bit output named `segs_n`. The outputs represent the seven-segment signals, the anode signal and the decimal point signal respectively.

This module generated the anode signal and also contains an instance of the sub module named `sevensseg_ext_n`. Since we are driving only the last digit, we could make the output as simple as `an_n = 8'b11111110`.

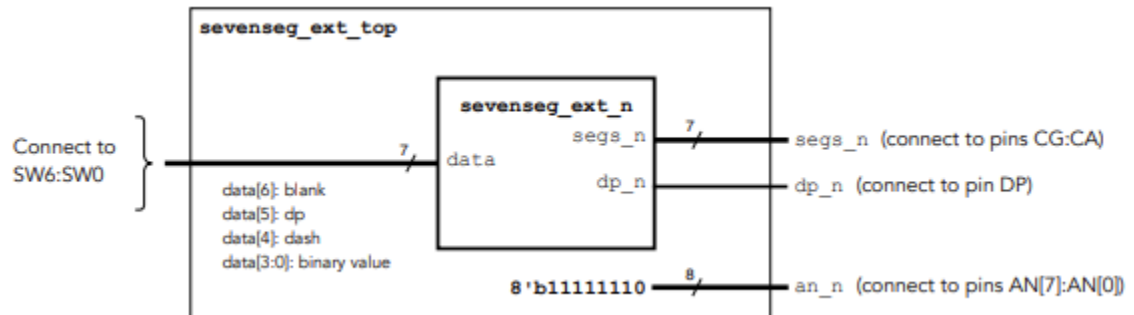- The diagram for the top module is shown below



- The `sevensseg_ext` module contains the design to drive the seven segments. It consists of a seven-bit input `d`. The function of each bit is described below.
  1. `d [6]` (blank) – when asserted, all output segments and the decimal point are turned off (i.e., to logic high).
  2. `d [5]` (dp) – when asserted (and blank is not asserted), assert output `dp_n` low to display the decimal point.
  3. `d [4]` (dash) – when asserted (and blank is not asserted), assert output `segs_n` display a dash/minus sign.
  4. `d [3:0]` (data) – when blank and dash are not asserted, assert output `segs_n` to display a seven-segment digit corresponding to the value of `data` for values 0-9. When the value of `data` is 10, 11, 12 and 15, the `segs_n` should display A, C, F and P respectively.
- We used multiplexers (if statement in Verilog) to test for the conditions when any of the first three bit are asserted and a decode to decode (case statement in Verilog) the outputs for `segs_n`.

 

### 3. Design realization:

- The design was realized by specifying the constraints for the switches and seven-segment display in an XDC file. The design was synthesized and bitstream generated for programming the board.

Results:

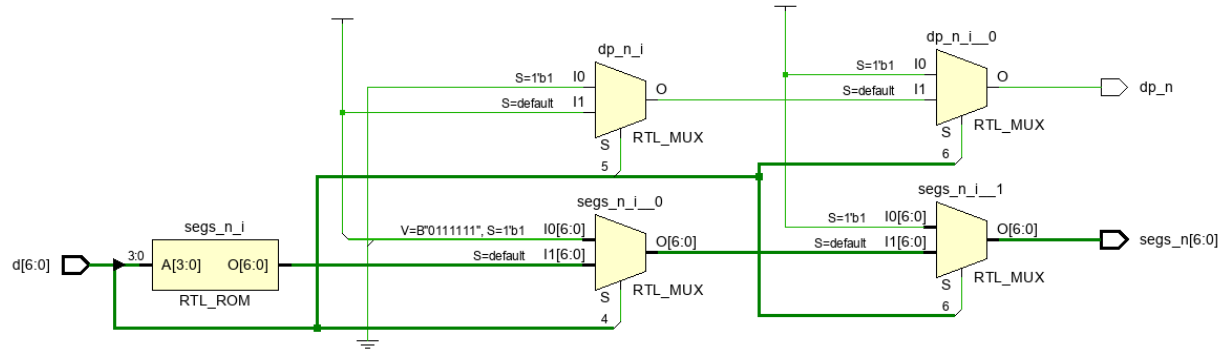


Figure 1schematic diagram for sevenseg\_ext

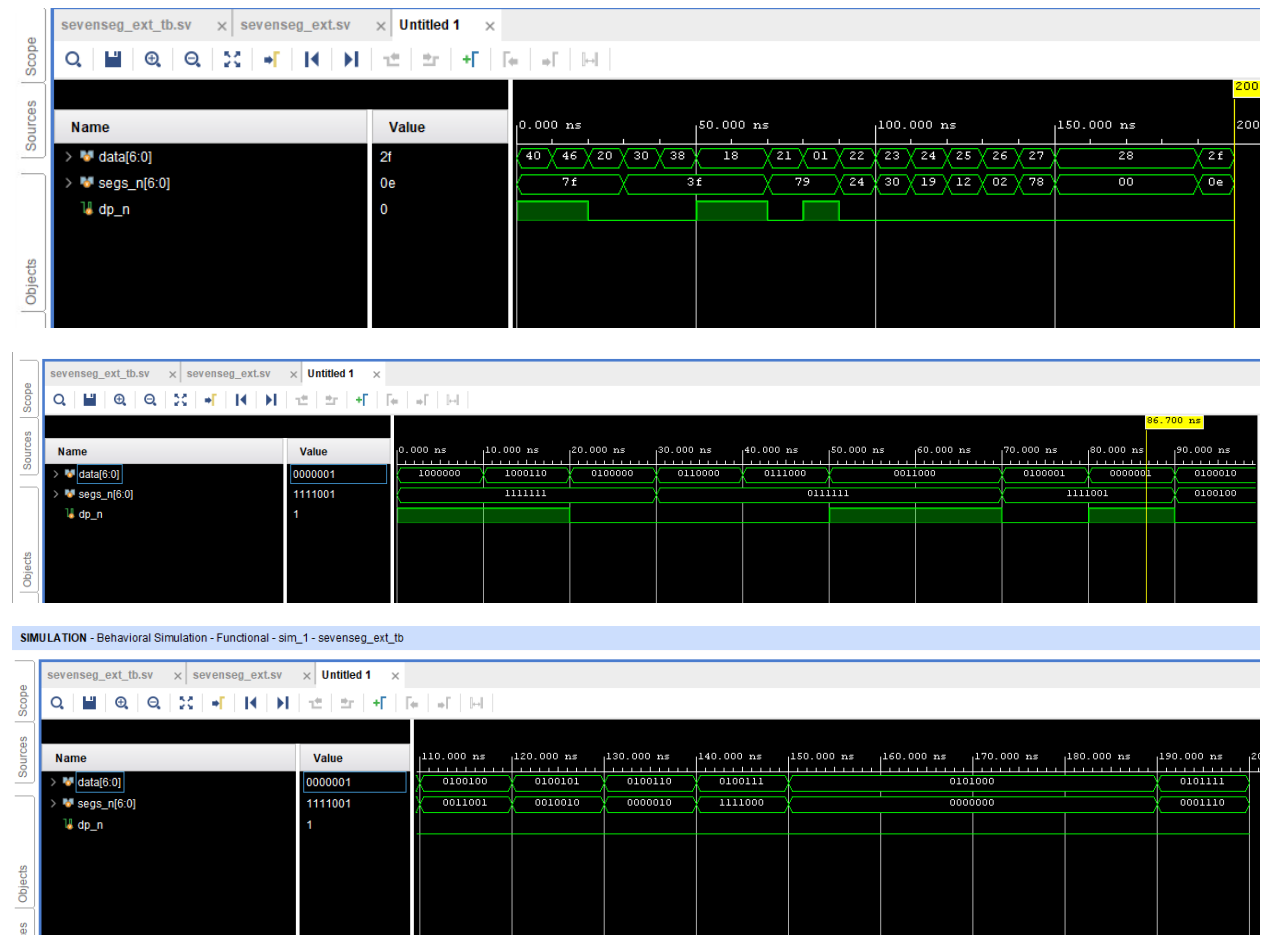


Figure 2simulation scope for sevenseg\_ext\_tb

The simulation scope diagrams show that the design is functioning as intended. For example when the first bit of the input is 1 , then all the bits of segs\_n should be actively high i.e 11111111.

**Conclusion:**

The design was pretty simple to implement. However, because we had come from a long break it took some time to familiarize with system Verilog again.

**Time spent on lab**

4 hrs

**N/B this lab was done by Hayes and Maurice in the first week before we switched partners**